



# The "Beatamp"

by V. E. HOLLEY

*This little amplifier has many applications, these ranging from standard workshop use to amplification of transistor radios. Both circuit and construction are simple, and the article also gives details of a suitable cabinet in which the amplifier and its speaker may be housed*

taken with confidence by anyone having an elementary knowledge of the subject and a small soldering iron. The components are few, and many readers will no doubt find all they want in the spares box.

### Circuit

Fig. 1 shows the circuit. The signal to be amplified is fed into the miniature jack socket, J<sub>1</sub>, and through the isolating capacitor C<sub>1</sub> to the volume control, and is then applied to the grid of the first valve. This is a high gain pentode, type EF91. Though the EF91 is really an r.f. amplifier, it is a versatile performer and will be found to work very well at audio frequencies in the circuit shown. The usual anode, screen and cathode bias resistors and capacitors are provided and, additionally, there is in the cathode circuit a small resistor, R<sub>4</sub>, of which more later.

**T**HIS IS A SIMPLE LITTLE AMPLIFIER WHICH WAS built originally for service on the workshop bench, but which was later appropriated by the teenage members of the family to amplify the output from a pocket transistor radio. In this service it earned its name and a great deal of popularity. Construction is quite simple and can be under-

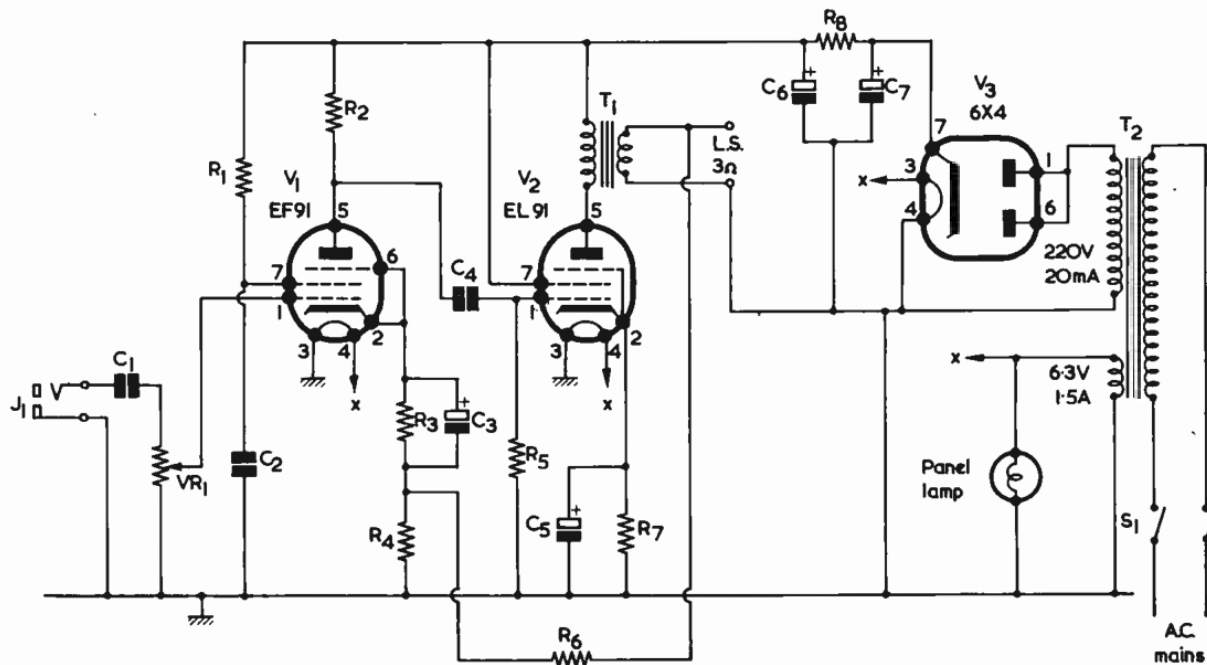


Fig. 1. The circuit of the "Beatamp"

### Resistors

(All fixed values  $\frac{1}{2}$  watt 10% unless otherwise stated)

R <sub>1</sub>	1.2M $\Omega$
R <sub>2</sub>	220k $\Omega$
R <sub>3</sub>	2.2k $\Omega$
R <sub>4</sub>	33 $\Omega$
R <sub>5</sub>	470k $\Omega$
R <sub>6</sub>	470 $\Omega$
R <sub>7</sub>	680 $\Omega$
R <sub>8</sub>	2k $\Omega$ , 2 watts
VR <sub>1</sub>	500k $\Omega$ potentiometer, log track

### Capacitors

C <sub>1</sub>	0.01 $\mu$ F, 350V wkg.
C <sub>2</sub>	0.1 $\mu$ F, 350V wkg.
C <sub>3</sub>	25 $\mu$ F electrolytic, 12V wkg.
C <sub>4</sub>	0.01 $\mu$ F 350V wkg.
C <sub>5</sub>	25 $\mu$ F electrolytic, 25V wkg.
C <sub>6</sub>	32 $\mu$ F electrolytic, 350V wkg.
C <sub>7</sub>	16 $\mu$ F electrolytic, 350V wkg.

### Transformers

T <sub>1</sub>	Speaker transformer, 70:1 or 80:1
T <sub>2</sub>	Mains transformer. Secondaries, 220V 20mA, 6.3V 1.5A.

### Valves

V <sub>1</sub>	EF91
V <sub>2</sub>	EL91
V <sub>3</sub>	6X4

### Switch

S <sub>1</sub>	d.p.s.t. rotary toggle switch
----------------	-------------------------------

### Jack Socket

J <sub>1</sub>	Miniature jack socket
----------------	-----------------------

### Loudspeaker

3 $\Omega$  elliptical loudspeaker, 7 $\times$ 4ins

### Miscellaneous

Pilot lamp, 6.3V 0.3A  
Pilot lamp holder  
3 B7G valveholders  
2 miniature jack plugs  
2 control knobs  
Insulated anchor tag  
2ft screened cable  
Flex for mains lead  
 $\frac{3}{8}$ in grommet  
Aluminium for chassis  
Wire, bolts, nuts, etc.

The amplified signal is passed by way of capacitor C<sub>4</sub> to the grid of the output valve, V<sub>2</sub>. This is a small power pentode having an output of 1.4 watts, which is fed to the 3 $\Omega$  loudspeaker by way of output transformer T<sub>1</sub>. As the anode current is only 16mA, quite a small transformer can be used and, for the best results, it ought to have a ratio of 70 or 80 to 1. Negative voltage feedback is usually associated with Hi-Fi circuits, but it

COMPOZETS

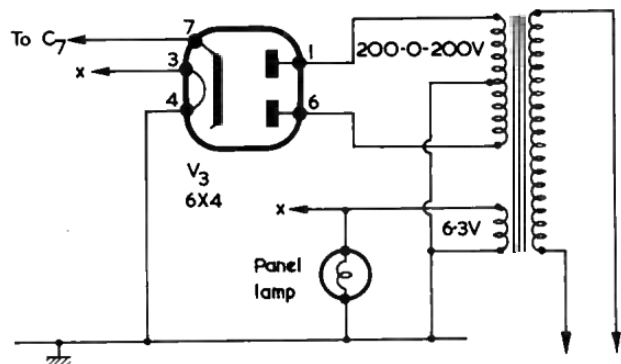


Fig. 2. An alternative power supply using full-wave rectification

is worth including in any amplifier because it improves the frequency response and reduces residual hum and the less desirable distortion introduced by the pentode output valve. A feedback voltage is accordingly taken from the output transformer secondary through resistor R<sub>6</sub> to the junction of R<sub>3</sub> and R<sub>4</sub>. The relative values of resistors R<sub>4</sub> and R<sub>6</sub> determine the proportion of the output voltage to be fed back.

### Power Supply

The power requirement is very modest and a small mains transformer able to provide 220V 20mA and 6.3V 1.5A is quite adequate. Half-wave rectification is given by a 6X4, but a metal rectifier or silicon diode will do just as well provided it has a peak inverse voltage (p.i.v.) rating of not less than 800. The end of the diode or rectifier marked red, or with a + sign, is the equivalent of the valve cathode. If the transformer has a full wave h.t. secondary winding, it is better to use full-wave rectification by valve and Fig. 2 shows how this should be arranged.\* A 200-0-200 volt secondary will be adequate here.

If the mains transformer primary has taps for different mains voltages, connect to the tap corresponding to the mains voltage to be used. With transformers having lead-out wires, primary taps which are not used should be carefully taped up to prevent short-circuits to adjacent conductors or the chassis. *Do not be tempted to dispense with the double-wound mains transformer in favour of a circuit in which the mains connects direct to chassis because, apart from the shock hazards associated with such a circuit, this will make the a.f. input connections live.*

The mains input is switched on and off by the rotary double pole switch, S<sub>1</sub>. Resistor R<sub>8</sub> and

\* At 200 volts r.m.s., the 6X4 should have a limiting resistance of 240 $\Omega$  in series with each anode. With a small mains transformer, this will normally be given by the resistance of the windings themselves. In Fig. 2, the resistance of either half of the h.t. secondary, plus the resistance of the primary, should be 240 $\Omega$  or more. If less, insert physical resistors, to make the total resistance up to this value, in series with each anode. In Fig. 1, the resistance of the h.t. secondary plus the resistance of the primary should, preferably, be 280 $\Omega$  or more. If less, insert a physical resistor, to make the total resistance up to this value, between the h.t. secondary and the anodes.—Editor.



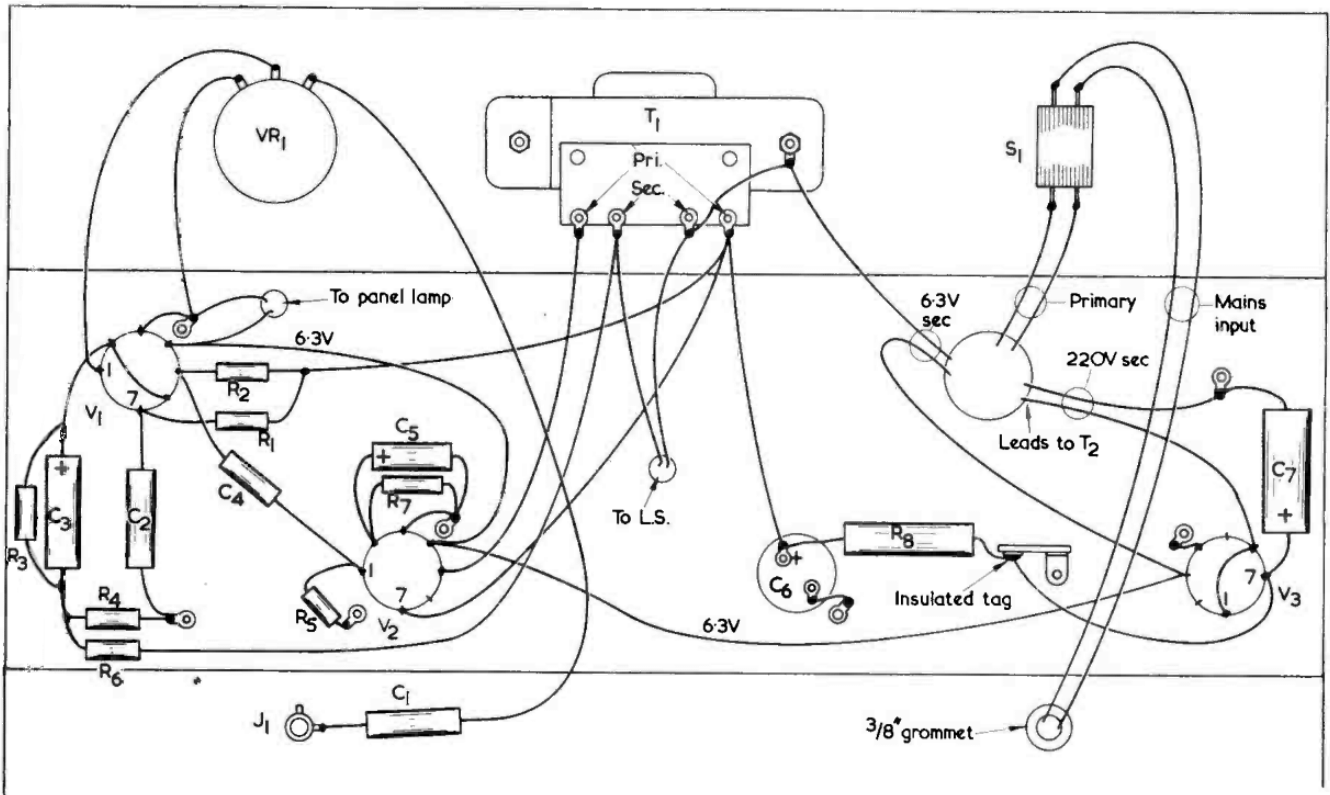


Fig. 4. Details of the wiring. The tag layout shown for speaker transformer  $T_1$  applies to the component employed in the prototype; other transformers may have a different tag layout and the connections shown here should be modified accordingly

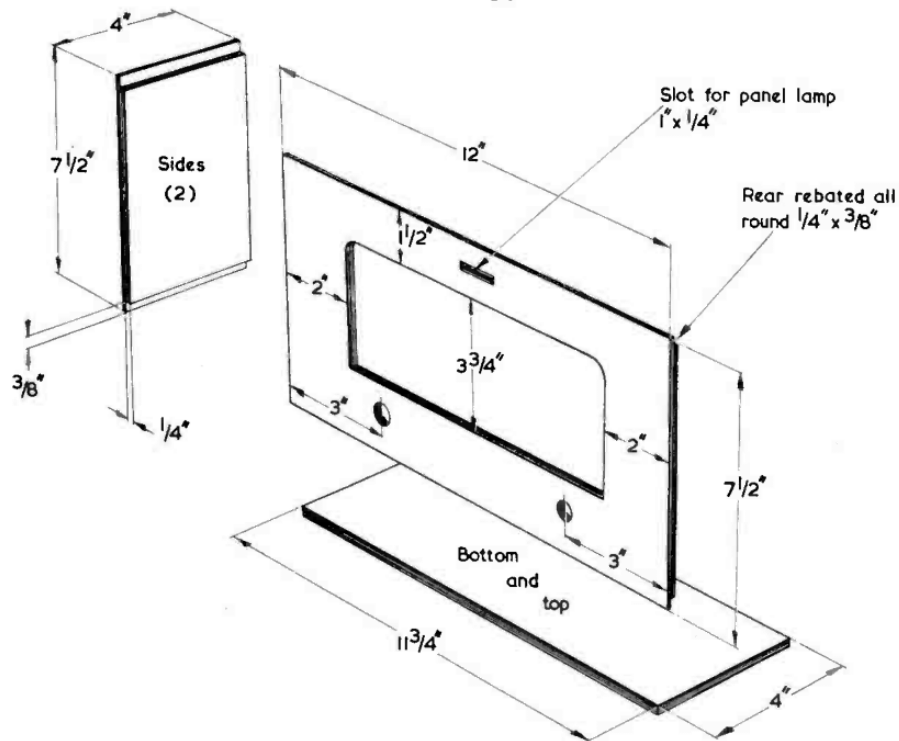


Fig. 5. Making a cabinet for the "Beatamp". The material is faced plywood  $\frac{3}{8}$  in thick. The spindle holes may be marked out from the chassis

be given with the *positive* meter lead to chassis.

If all is well, power may be applied. The speaker should, of course, be connected.

As the "Beatamp" warms up, it will scream disrespectfully at the constructor if the feedback happens to be positive. Do not reproach yourself—even the experts cannot predict the right connection. Switch off nonchalantly and with a flourish of the soldering iron, reverse the connections to the primary of the output transformer to make the feedback negative.

### Operation

It remains to make up a screened lead about 2ft long with a miniature jack plug at each end. Insert one plug into the "Beatamp" and the other into the socket provided for the earpiece in a transistor receiver and all is set for the Big Beat. If the current consumption of the receiver varies with the setting of the volume control, battery life can be prolonged by using a low setting and bringing the signal up to the desired level in the "Beatamp".

### Cabinet

Upon promotion to domestic service, the prototype, which had hitherto rested naked upon the bench, was given the plywood cabinet shown in the illustration. Details of the measurements and method of construction are given in Fig. 5. Faced plywood  $\frac{3}{8}$ in thick is very suitable material. The

joints can be secured very satisfactorily with panel pins and glue and quite a good exterior finish can be produced by staining and varnishing. The original was french polished, but this was not observed to improve the performance!

A rectangular slot was provided in the front panel for the pilot lamp. The speaker aperture should be covered with Tygan or some similar material, secured with impact adhesive. The 7×4in loudspeaker should first be fitted to a piece of  $\frac{1}{2}$ in hardboard in which a suitable aperture has been cut and the whole fitted into the cabinet with wood screws.

To make the securing holes for the chassis, first clamp it in position. Then drill upwards, through the bottom of the cabinet and through the end flanges of the chassis, two holes, one at each end. If the holes in the wood are then enlarged and wood screws of suitable size inserted, they will have a selftapping action as they enter the aluminium and will keep the chassis very firmly in position. The panel lamp slot can be covered with a piece of coloured Perspex or even paper, and the lamp holder secured in position with a small wood screw.

A carrying handle at the top of the cabinet is a useful addition and four small pieces of rubber to act as feet, secured to the bottom with Evostick, will avoid scratches on any polished surface on which the unit may stand.