

Described by W. Holmes

This article gives full constructional details of an inexpensive amplifier which is capable of a very high performance level

DESPITE THE FACT THAT PRESENT-DAY audio amplifying and reproducing equipment tends to be centred on complex and relatively costly amplifiers there is a very considerable demand amongst constructors for amplifiers which, whilst being capable of offering a high performance level, are smaller and less expensive. The Cooper-Smith "Bantam" falls into this category, and it has been designed to give a quality of reproduction which is considerably in advance of that provided by standard radios and radiograms. The "Bantam" possesses all the features normally found in much more complex equipment: it has continuously variable bass and treble controls, it contains its own mains power unit, it can provide heater and h.t. power for ancillary equipment such as f.m. tuner units and the like, and it is capable of driving speakers at either 15Ω or 3.75Ω impedance. The output stage is single-ended, the output valve specified being rated at a high power figure. This valve works into an output transformer having a generously heavy core,

negative feedback from its secondary being applied to the stage preceding the output valve.

As may be seen from the photograph at the head of this article, the completed amplifier presents a very neat and professional appearance. A separate escutcheon, also shown in the photograph, enables the amplifier to be mounted in a cabinet, if desired, the control spindles protruding through the escutcheon.

Technical features for the "Bantam" are as follows:

- Power Output: 3-4 watts.
- Frequency Response: 40-25,000 c/s \pm 1dB at 1 watt (tone controls flat).
- Tone Controls: Bass and treble cut and boost, continuously variable.
- Output Impedances: 3.75Ω and 15Ω .
- Input Sensitivity: 60mV for 3 watts output.
- Valves: ECF80, EL84 (or 6BQ5), EZ81.
- Spare Power: 250V at 45mA, 6.3V at 2A.
- Weight: 8 $\frac{1}{2}$ lb.
- Size: 8 x 6 $\frac{1}{2}$ x 4 $\frac{1}{2}$ in.

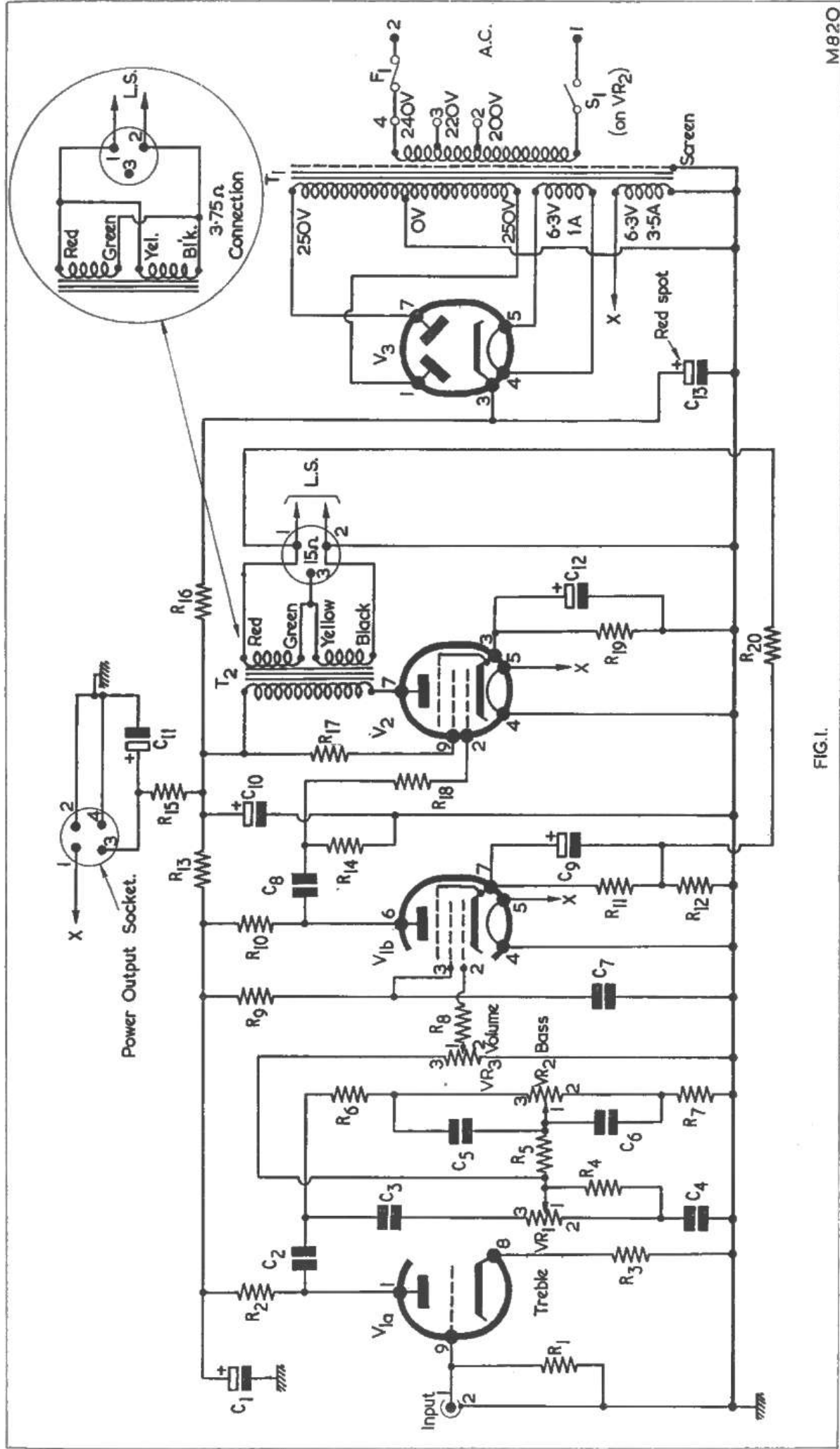


FIG.1.

Fig. 1. The theoretical circuit of the Cooper-Smith "Bantam". The identification numbers on potentiometers and sockets apply to the similarly numbered tags in Fig. 2

M820

The Circuit

The circuit of the Bantam appears in Fig. 1. The input signal is applied to the grid of $V_{1(a)}$, this being the triode section of an ECF80. $V_{1(a)}$ functions as a triode voltage amplifier and compensates for the loss of signal voltage occurring in the subsequent tone control circuit. A small degree of current negative feedback is applied to the input stage by means of the un-bypassed cathode resistor R_3 .

to the pentode section, $V_{1(b)}$ of the ECF80.

The pentode also functions as a voltage amplifier, the amplified signal appearing across its anode load, R_{10} . Due to the choice of valve and operating conditions, $V_{1(b)}$ anode has a relatively low impedance to chassis. The anode of $V_{1(b)}$, working at this relatively low impedance, then drives the grid of the output valve, V_2 , via the grid stopper, R_{18} .

The output valve functions in conventional

Components List

Resistors

R_1	$1M\Omega$	$\frac{1}{8}W$	20%
R_2	$100k\Omega$	$\frac{1}{2}W$	20%
R_3	$1.2k\Omega$	$\frac{1}{4}W$	20%
R_4	$47k\Omega$	$\frac{1}{8}W$	20%
R_5	$39k\Omega$	$\frac{1}{4}W$	20%
R_6	$68k\Omega$	$\frac{1}{4}W$	20%
R_7	$6.8k\Omega$	$\frac{1}{4}W$	20%
R_8	$1k\Omega$	$\frac{1}{8}W$	20%
R_9	$470k\Omega$	$\frac{1}{4}W$	20%
R_{10}	$100k\Omega$	$\frac{1}{4}W$	20%
R_{11}	$1.8k\Omega$	$\frac{1}{4}W$	20%
R_{12}	100Ω	$\frac{1}{4}W$	20%
R_{13}	$22k\Omega$	$\frac{1}{2}W$	20%
R_{14}	$1M\Omega$	$\frac{1}{4}W$	20%
R_{15}	See text		
R_{16}	470Ω	5W	20%
R_{17}	100Ω	$\frac{1}{4}W$	20%
R_{18}	$10k\Omega$	$\frac{1}{8}W$	20%
R_{19}	150Ω	$\frac{1}{2}W$	20%
R_{20}	For 15Ω output $22k\Omega$ $\frac{1}{4}W$ 20% For 3.75Ω output $10k\Omega$ $\frac{1}{4}W$ 20%		

Condensers

C_1	$16\mu F$	275 W.V.	Daly
C_2	$0.02\mu F$	350 W.V.	static
C_3	$560pF$	silver mica,	R.B.S.
C_4	$8,000pF$	silver mica,	R.B.S.
C_5	$2,000pF$	silver mica,	R.B.S.
C_6	$0.02\mu F$	Moldseal	
C_7	$0.1\mu F$	350 W.V.	Static
C_8	$0.05\mu F$	350 W.V.	Static
C_9	$50\mu F$	12 W.V.	Daly
C_{10}, C_{13}	$50+50\mu F$,	350 W.V.,	with clip, Daly

C_{11}	$8\mu F$	350 W.V.	Daly
C_{12}	$50\mu F$	25 W.V.	Daly

Potentiometers

VR_1	$250k\Omega$	Log.,	A.B. Metal
VR_2	$250k\Omega$	Log with	switch
VR_3	$1M\Omega$	Log.,	A.B. Metal

Valves

V_1	ECF80
V_2	6BQ5 or EL84
V_3	EZ81

Miscellaneous (all available from H. L. Smith & Co. Ltd.)

T_1	Mains Transformer, 250-0-250V 100mA 6.3V 3.5A, 6.3V 1A
T_2	Output Transformer, Electro-Voice D91
	Valveholder B9A (2)
	Valveholder B9A with skirt (1)
	Mains plug and socket, Bulgin
	Speaker plug and socket (3-pin), Cinch
	Power output plug and socket (4-pin), Cinch
	Input plug and socket, coaxial
	Mains selector, fused 2A
	Tagstrips, 12-way (pair)
	Wire, sleeving, screws, nuts
	Chassis, punched, bronze
	Control panel, gold hammered
	Control knobs, gold insert (3)

The signal on the anode of $V_{1(a)}$ is fed to the tone control circuit around potentiometers VR_1 and VR_2 . This circuit¹ is one which has been well-proven in practice, and was successfully incorporated in the Cooper-Smith Mark II Control Unit.² The output from the tone control circuit is applied to the upper terminal of VR_3 , the volume control; the signal level tapped off by the slider of this control being fed, via the grid-stopper R_8 ,

manner, feeding into the speaker transformer T_2 , the secondary of which connects to the loudspeaker output socket. In the main circuit diagram the two secondary windings are connected in series, thereby offering an output impedance of 15Ω . In the "inset", the secondary windings are connected in parallel, offering an output impedance of 3.75Ω .

Negative feedback is obtained from the secondary of the speaker transformer via R_{20} . This resistor, with R_{12} , forms a fixed potentiometer which causes a proportion of the secondary output voltage to be injected

¹ "Design for a Pre-Amplifier", D. H. W. Busby, *Wireless World*, July 1955.

² "The Cooper-Smith Mark II Control Unit", J. Cooper, *The Radio Constructor*, February, 1958.

into the cathode of $V_{1(b)}$. For 15Ω output operation R_{20} has a value of $22k\Omega$. For 3.75Ω output operation (in which half the signal voltage given for 15Ω operation is available across the secondary of T_2) R_{20} has a value of $10k\Omega$.

H.T. power in the "Bantam" is obtained by means of a mains transformer having a full wave h.t. secondary, rectification being provided by V_3 . V_3 cathode connects into the filter components C_{13} , R_{16} , and C_{10} , the output valve, V_3 , obtaining its h.t. supply from the smoothed voltage appearing across the latter condenser. Further smoothing is provided by R_{13} and C_1 , the voltage across C_1 being employed for $V_{1(a)}$ and $V_{1(b)}$.


The power supply has been designed to provide an h.t. output of 250 volts at a maximum current of 100mA. The amplifier current requirement is 55mA only, with the result that an h.t. voltage of 250, with a maximum current of 45mA, becomes available for ancillary equipment such as radio tuners, etc. Such equipment may obtain h.t. and heater power from the power output

socket shown in Fig. 1. Since individual requirements may vary, a value for the h.t. series resistor, R_{15} , has not been specified; this being chosen to suit the particular needs of the equipment envisaged. If, to take an example, the ancillary equipment were to require an h.t. supply of 200 volts at 40mA, then R_{15} would be required to drop 50 volts (from the 250 volts available in the amplifier)

at this current. From Ohms Law $R = \frac{E}{I}$ the required value for R_{15} under these circumstances would be $\frac{50}{0.04} = 1,250\Omega$. Should

the amplifier be purchased in kit form, either the value for R_{15} , or the voltage and current requirements of the associated equipment, should be specified.

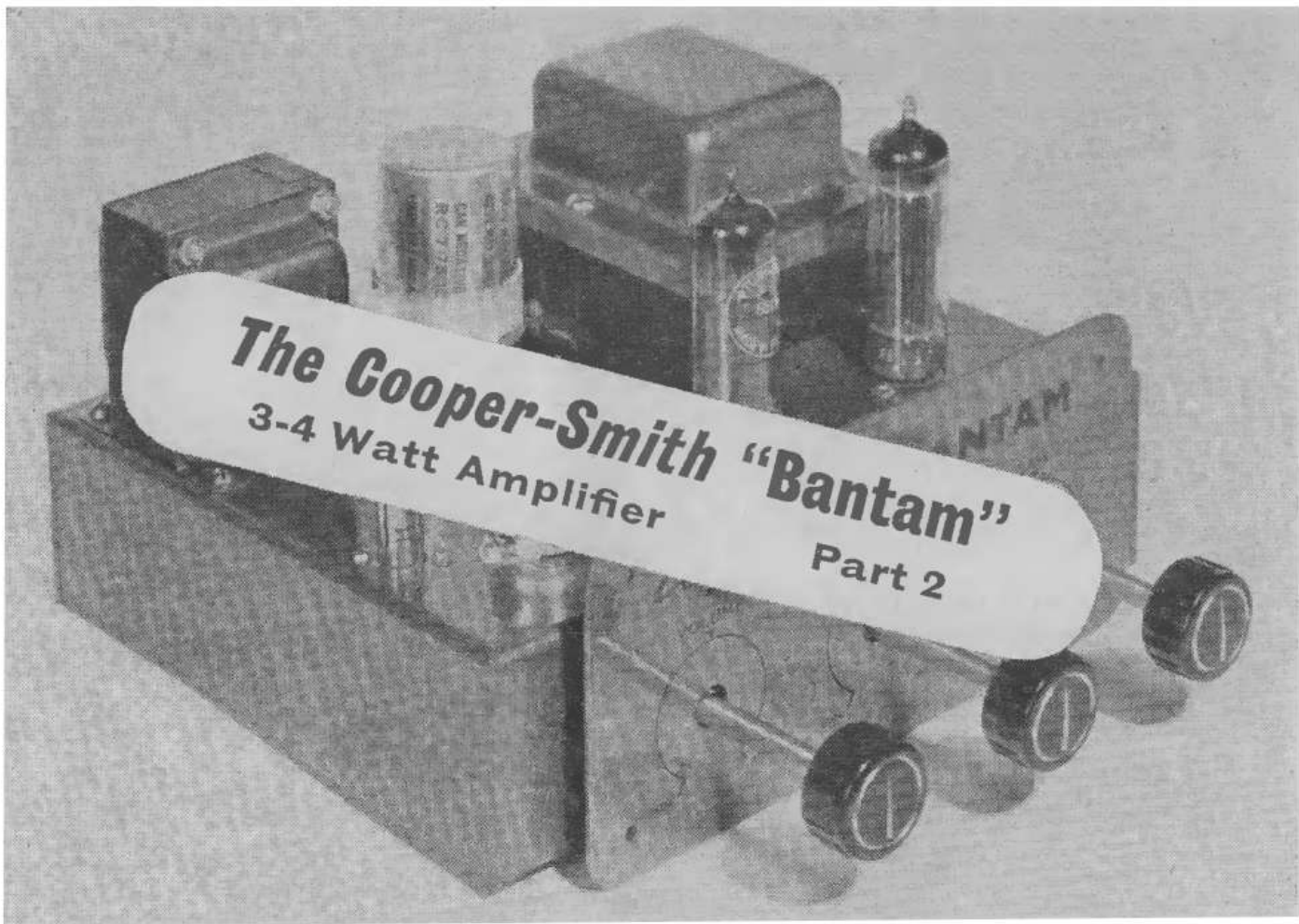A 6.3V heater supply is also available at the power output socket, this being obtained from the same heater winding of the mains transformer which feeds the heaters of $V_{1(a)}$, $V_{1(b)}$, and V_2 . The heater current available at the socket is 2A.



Described by W. Holmes

This concluding article gives full constructional details of an inexpensive amplifier which is capable of a very high performance level

Construction

Construction of the Cooper-Smith "Bantam" is a relatively simple procedure. The photographs accompanying this article show very clearly the clean and neat layout employed, and they will be of assistance during the process of mounting components and wiring up. A layout and wiring diagram is given in Fig. 2, this showing the position of all components and connections. It will be noted, in Fig. 2, that individual tags on potentiometers, valveholders, sockets and the mains voltage selector panel are numbered. These numbers correspond to those appearing in the circuit diagram of Fig. 1. Also shown numbered are the tags on the two 12-way tagstrips. All these tags are referred to by their numbers in the step-by-step instructions which follow. The rear apron of the chassis in Fig. 2 is shown opened out in order that connections made to the components mounted on it may be illustrated more clearly.

Step-by-Step Instructions

Construction proceeds as follows:

1. Fit the mains socket, mains selector panel, power output socket and speaker socket to the rear apron. All these are fitted from the inside except for the mains socket.

2. Fit the mains transformer T_1 , ensuring that its tags take up the position shown in Fig. 2. Also, fit the speaker transformer T_2 , bringing its leads out as shown in Fig. 2. It is necessary for the lower right-hand nut (adjacent to the tag—fitted later—numbered 23 in Fig. 2) to make good contact to chassis. Ensure good contact by scraping, or cleaning, the underside of the chassis before this nut is fitted.

3. Fit the dual condenser C_{10} , C_{13} , ensuring that the tag marked red is nearest the mains transformer T_1 . Make certain of good chassis contact to the condenser clip by scraping the underside of the chassis at the points where the mounting nuts tighten down.

4. Fit the input socket, ensuring correct orientation (its earthy tag, 2, should take up the position shown in Fig. 2). Again, scrape the chassis to ensure good contact to its mounting nuts.

5. Fit the valveholders, ensuring correct orientation. Note that V_1 valveholder has a

contact) to the hole near V_2 . (R_{18} —fitted later—is above this hole in Fig. 2.) Mount the two 12-way tagstrips as shown in Fig. 2. The lower tagstrip is mounted over the 6BA bolt just fitted, and over the outside bolt securing the input socket. The upper tagstrip is mounted over the lower right hand

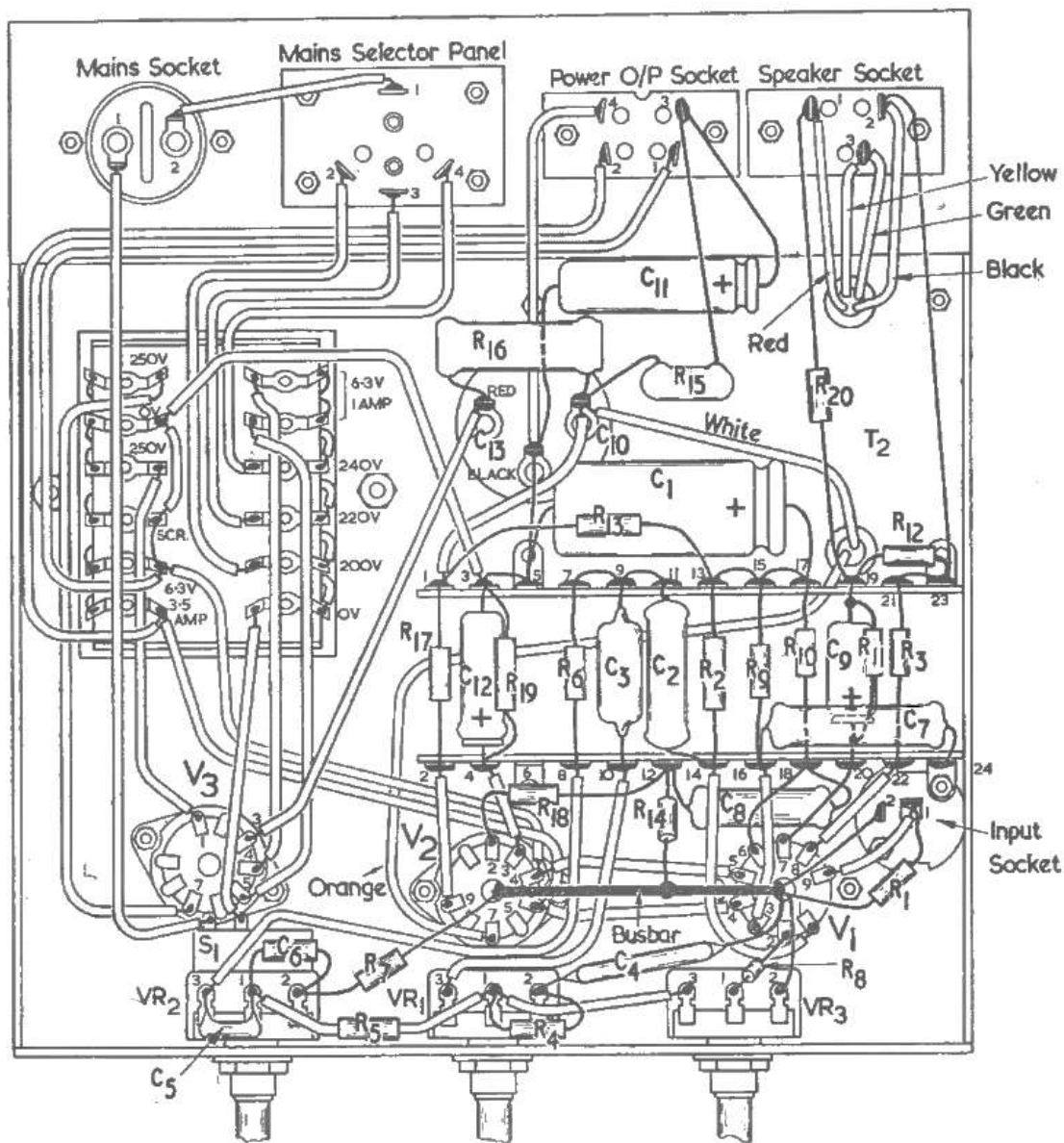


FIG.2.
Layout and Wiring Diagram.

M821


Fig. 2. Layout and wiring diagram. The rear apron of the chassis is laid flat to show the connections to the rear sockets and the mains selector panel more clearly

skirt (see photographs) and is mounted above the chassis, and that V_2 and V_3 valveholders are mounted below. Scrape the chassis to ensure good contact to the securing nuts for V_1 valveholder.

6. Fit a 6BA nut and bolt (again scraping the underside of the chassis to give good

bolt securing the speaker transformer (referred to in step 2) and the lower bolt securing the dual condenser C_{10} , C_{13} . Both tagstrips are mounted over the nuts which have previously been tightened, and are secured by fitting additional nuts.

7. Fit the three potentiometers VR_1 , 2

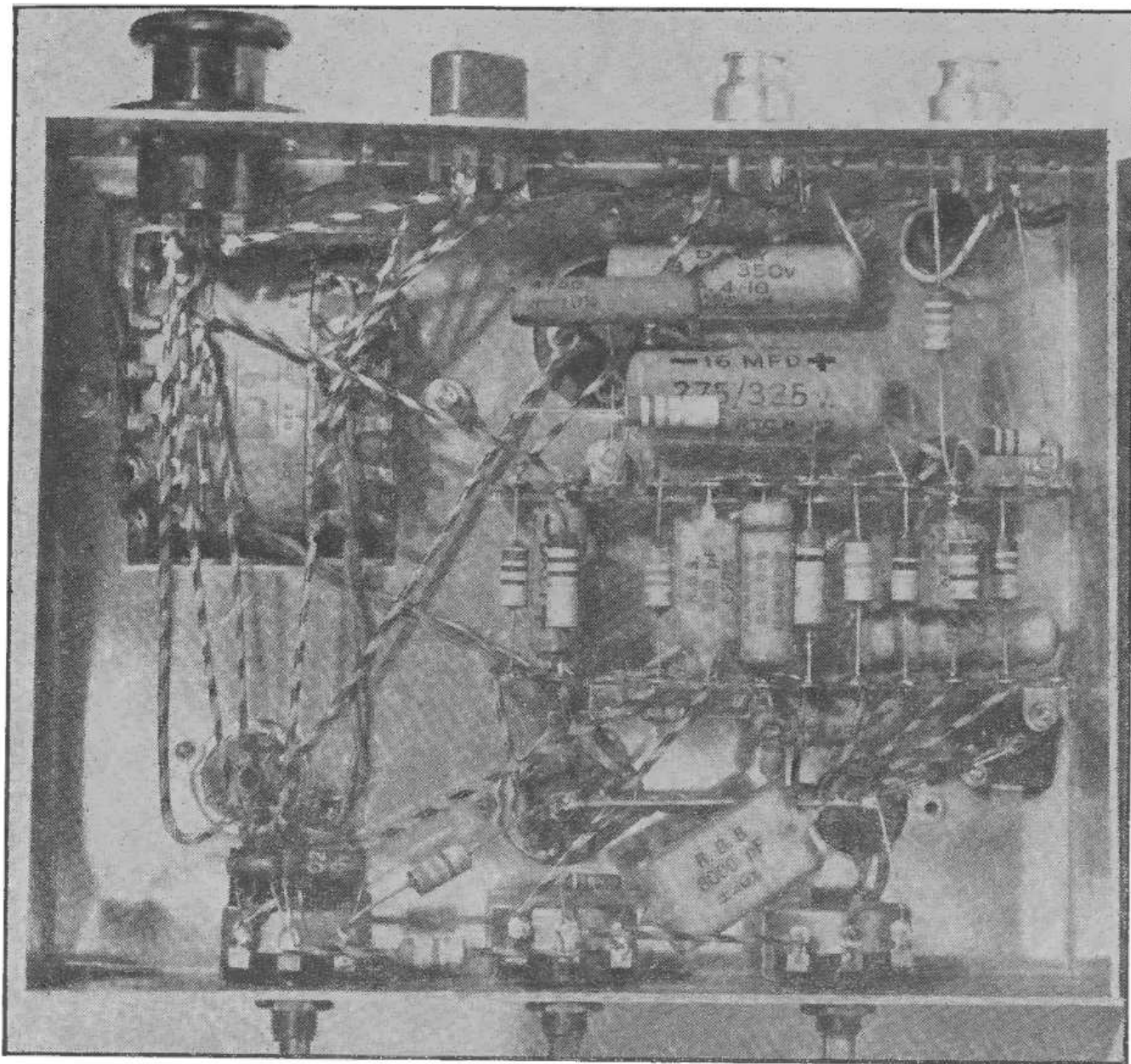

Under-chassis view of the "Bantam". This view, which demonstrates the clean wiring layout, may be compared with Fig. 2

and 3, to the front panel as shown in Fig. 2 (noting the locating holes in the chassis).

Wiring Up

Wiring up now commences. In order that all connections may be made to each individual tag before they are soldered to that tag, soldering should only be carried out where stated.

8. Using twisted wiring, connect in parallel pins 4 and 5 of V_1 , pins 4 and 5 of V_2 , the 6.3V 3.5A tags on T_1 , and tags 1 and 2 on the power output socket. Solder all these joints except the 6.3V 3.5A tag on T_1 adjacent to the "SCR" tag. Also using twisted wiring, connect in parallel, and solder, pins 4 and 5 of V_3 and the 6.3V 1A tags on T_1 . (Fig. 2 shows this wiring step with untwisted wire for ease of circuit tracing.)

9. Carefully following Fig. 2, connect the 6.3V 3.5A tag on T_1 adjacent to the "SCR" tag to that tag, carrying on to the 0V tag (h.t. secondary) on T_1 , and to tag 3 of the tagstrips. Solder all joints except tag 3.

10. Carefully following Fig. 2, connect 0V tag (mains primary) on T_1 , to one tag of switch S_1 and solder. Connect 200V tag on T_1 to tag 2 of mains selector panel and solder. Connect 220V tag on T_1 to tag 3 of mains selector panel and solder. Connect 240V tag on T_1 to tag 4 of mains selector panel and solder. Connect the two 250V tags on T_1 to pins 1 and 7 of V_3 and solder.

11. The speaker transformer, T_2 , is next connected into circuit. Connect its orange lead (following route in Fig. 2) to pin 7 of V_2 and solder. Connect its white lead (following route in Fig. 2) to C10.

12. For 15 Ω output only. Connect red lead

of T_2 to tag 1 of speaker socket. Connect black lead of T_2 to tag 2 on speaker socket. Connect yellow and green leads to tag 3 on speaker socket, soldering at tag 3. These connections are shown in Fig. 2.

13. *For 3.75 Ω output only.* Connect red and yellow leads of T_2 to tag 1 on speaker socket. Connect green and black leads of T_2 to tag 2 on speaker socket. These connections are not shown in Fig. 2.

14. Tagstrip connections come next. Connect R_{17} (100 Ω) between tags 1 and 2.

15. Connect R_{19} (150 Ω) and C_{12} (50 μ F, 25 W.V.) between tags 3 and 4, observing correct polarity in C_{12} . Join tags 3 and 5. Solder tag 3.

16. Connect C_1 (16 μ F, 275 W.V.) between tags 5 and 17, observing correct polarity.

17. Connect R_6 (68k Ω) between tags 7 and 8.

18. Connect C_3 (560pF) between tags 9 and 10.

19. Connect C_2 (0.02 μ F) between tags 11 and 14. Join, and solder, tags 7, 9 and 11.

20. Connect R_2 (100k Ω $\frac{1}{2}$ W—as opposed to the $\frac{1}{4}$ W R_{10}) between tags 13 and 14.

21. Connect R_9 (470k Ω) between tags 15 and 16.

22. Connect R_{10} (100k Ω) between tags 17 and 18. Join tags 13, 15 and 17, soldering at 15 and 17.


23. Connect C_9 (50 μ F, 12 W.V.) and R_{11} (1.8k Ω) between tags 19 and 20, observing correct polarity of C_9 .

24. Connect R_3 (1.2k Ω) between tags 21 and 22.

25. Connect R_{12} (100 Ω) between tags 19 and 23. Join tags 21 and 23, soldering at 21.

26. Connect R_{13} (22k Ω $\frac{1}{2}$ W—as opposed to the $\frac{1}{4}$ W R_{20} when 15 Ω output is used) between tags 1 and 13, soldering at 13.

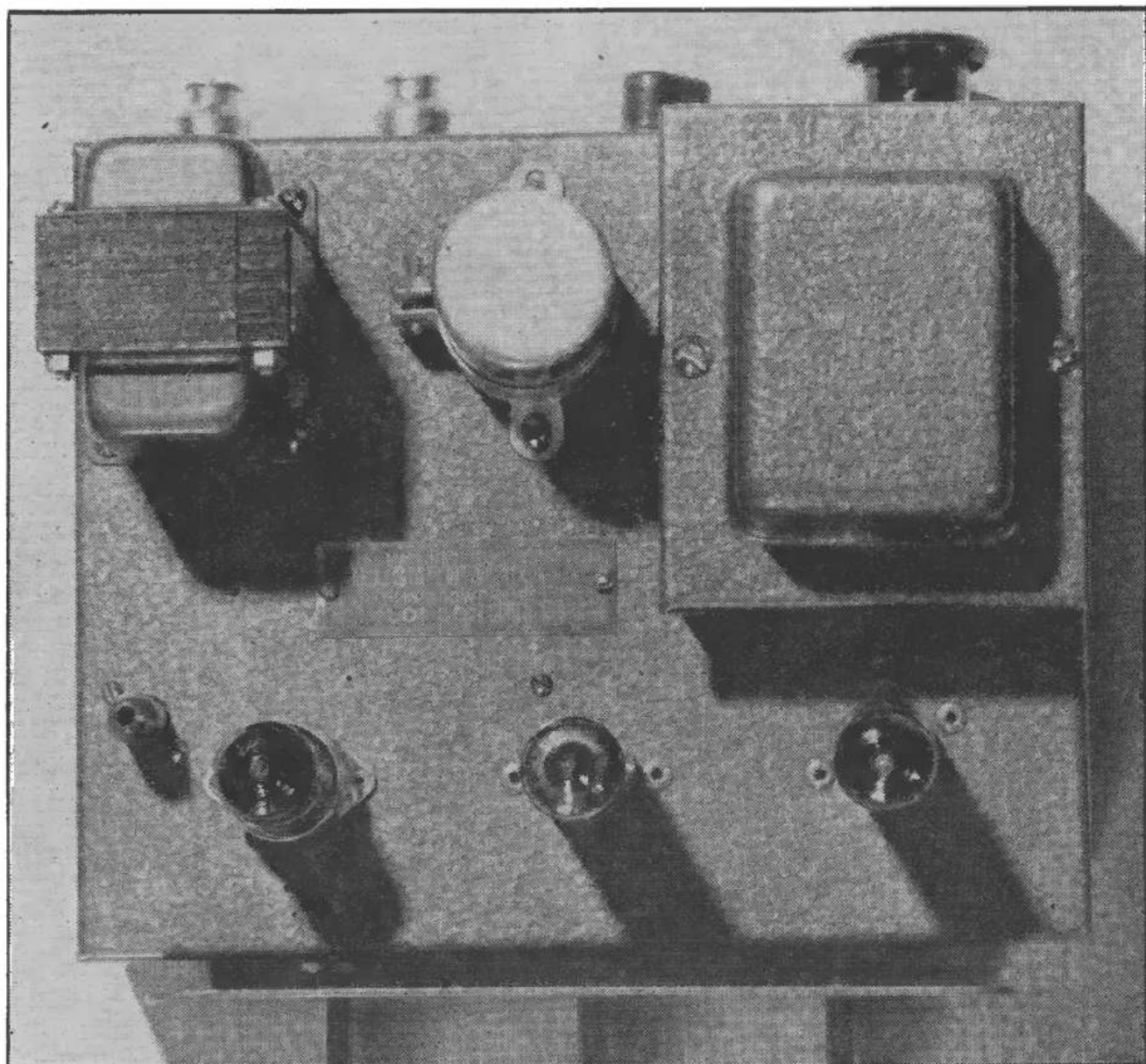27. Connect C_8 (0.05 μ F) between tags 12 and 18.



Top view of the chassis, illustrating its neat appearance. The rectifier, V_3 , is at the mains transformer end of the chassis, whilst V_2 is in the centre

28. Connect C_7 ($0.1\mu\text{F}$) between tags 16 and 24, soldering at 24.

29. The rest of the wiring is now continued. Following the route shown in Fig. 2, connect pin 3 of V_3 to C_{13} , soldering at pin 3.

30. Following Fig. 2, connect and solder the remaining tag of switch S_1 to tag 1 of the mains socket.

31. Connect and solder tag 2 of the mains socket to tag 1 of the mains selector panel.

32. Following Fig. 2, identify the negative (black) tag of C_{10} , C_{13} . All the following connections involve this tag. Connect the negative tag of C_{10} , C_{13} to tag 5 on the tagstrips, soldering at tag 5. Connect the negative tag of C_{10} , C_{13} to tag 4 on the power output socket, soldering at tag 4. Connect C_{11} ($8\mu\text{F}$, 350 W.V.) between the negative tag of C_{10} , C_{13} and tag 3 on the power output socket, observing correct polarity. Solder at negative tag of C_{10} , C_{13} .

33. Following Fig. 2, connect C_{10} to tag 1 on the tagstrips, soldering at tag 1.

34. Following Fig. 2, connect R_{16} (470Ω) between C_{10} and C_{13} , soldering at C_{13} .

35. Following Fig. 2, connect and solder R_{15} (value according to requirements—see above) between C_{10} and tag 3 on the power output socket.

36. Connect and solder R_{20} ($22\text{k}\Omega$ for 15Ω output, $10\text{k}\Omega$ $\frac{1}{4}$ watt, as opposed to the $\frac{1}{8}$ watt R_{18} , for 3.75Ω output) between tag 19 of the tagstrips and tag 1 on speaker socket.

37. Join, and solder, tag 23 of the tagstrips to tag 2 on speaker socket.

38. Join tag 1 on input socket to pin 9 of V_1 . Solder at pin 9.

39. Bend the supplied thick piece of wire at right angles, $\frac{3}{4}$ in in from each end, and solder to centre spigots of V_1 and V_2 to form a busbar between them. (The bent ends enter the spigots, and the busbar is shown in heavy line in Fig. 2.) All connections made to the busbar which follow are soldered at the busbar.

40. Join and solder pin 2 on the input socket to the busbar.

41. Connect and solder R_1 ($1\text{M}\Omega$ $\frac{1}{8}\text{W}$ —as opposed to the $\frac{1}{4}\text{W}$ R_{14}) between tag 1 of the input socket and the busbar.

42. Join and solder pin 8 of V_1 and tag 22 of the tagstrips.

43. Join and solder pin 7 of V_1 and tag 20 of the tagstrips. Use sleeving (omitted from Fig. 2 for clarity).

44. Join and solder pin 6 of V_1 and tag 18 of the tagstrips. Use sleeving (omitted from Fig. 2 for clarity).

45. Join and solder pin 3 of V_1 and tag 16 of the tagstrips.

46. Join and solder pin 1 of V_1 and tag 14 of the tagstrips.

47. Connect and solder R_8 ($1\text{k}\Omega$) between pin 2 of V_1 and tag 1 of VR_3 .

48. Connect R_{18} ($10\text{k}\Omega$) between pin 2 of V_2 and tag 12 of the tagstrips. Solder at pin 2.

49. Join and solder pin 3 of V_2 and tag 4 of the tagstrips.

50. Join and solder pin 9 of V_2 and tag 2 of the tagstrips.

51. Join tag 3 of VR_2 to tag 8 of the tagstrips, and solder at tag 8. Follow route shown in Fig. 2.

52. Join and solder tag 3 of VR_1 to tag 10 of the tagstrips. Follow route shown in Fig. 2.

53. Connect and solder R_{14} ($1\text{M}\Omega$) between tag 12 of the tagstrips and the busbar.

54. Connect C_5 ($2,000\text{pF}$) between tags 1 and 3 of VR_2 . Solder at tag 3.

55. Connect C_6 ($0.02\mu\text{F}$) between tags 1 and 2 of VR_2 .

56. Connect and solder R_7 ($6.8\text{k}\Omega$) between tag 2 of VR_2 and the busbar.

57. Connect R_5 ($39\text{k}\Omega$) between tag 1 of VR_2 and tag 1 of VR_1 . Solder at tag 1 of VR_2 .

58. Join tag 1 of VR_1 and tag 3 of VR_3 . Solder at tag 3.

59. Connect R_4 ($47\text{k}\Omega$) between tags 1 and 2 of VR_1 . Solder at tag 1.

60. Connect and solder C_4 ($8,000\text{pF}$) between tag 2 of VR_1 and the busbar.

61. Join and solder tag 2 of VR_3 to busbar.

62. Fit valves and knobs.

Operation

The Cooper-Smith "Bantam" is now complete and ready for operation.

The voltage selector panel should be set to the mains voltage with which the amplifier is to be used. The main input fuse (rating 2A) is housed in the bridging plug of the panel. The speaker should be connected to pins 1 and 2 of the speaker socket (tag 3 of this socket, used for the 15Ω output impedance connection, is an anchoring tag only).

The input sensitivity of the amplifier is 60mV for 3 watts output, and care should be taken to avoid applying excessive inputs. If the associated radio tuner or pick-up provides an output considerably in excess of 60mV it will be necessary for this to be attenuated before coupling to the amplifier. Suitable attenuation will normally be given by providing a pre-set potentiometer before the input socket, this being adjusted until a smooth control is provided by VR_3 . As a rough guide to the correct setting of such a potentiometer, the amplifier should begin to overload when VR_3 is some three-quarters advanced.