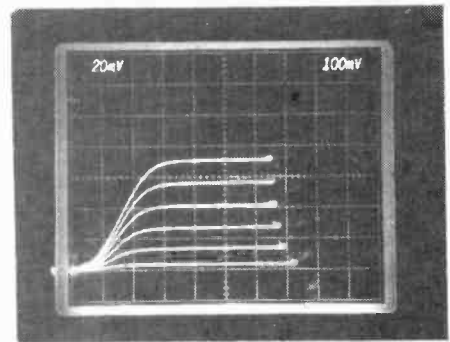



CURVE TRACER




Display the dynamic characteristics of a variety of semi conductor devices with out curve tracer. Design by J. H. Adams.

THE CURVES INVOLVED in this design are not unfortunately those of the Bardots and Welchs of this world but curves that, to some, are just as interesting. The design will allow the dynamic voltage-current characteristics of diodes and transistors to be displayed on the screen of a DC 'scope capable of taking an external X input.

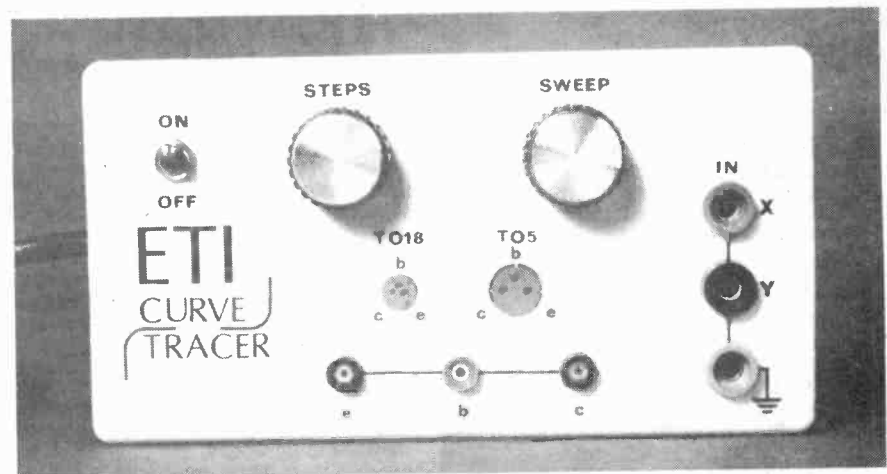The performance of the unit will not be up to that of a commercial machine but considering such commercial designs are priced in the thousand pound range while our design could be built for around five pounds, we're not doing too badly.



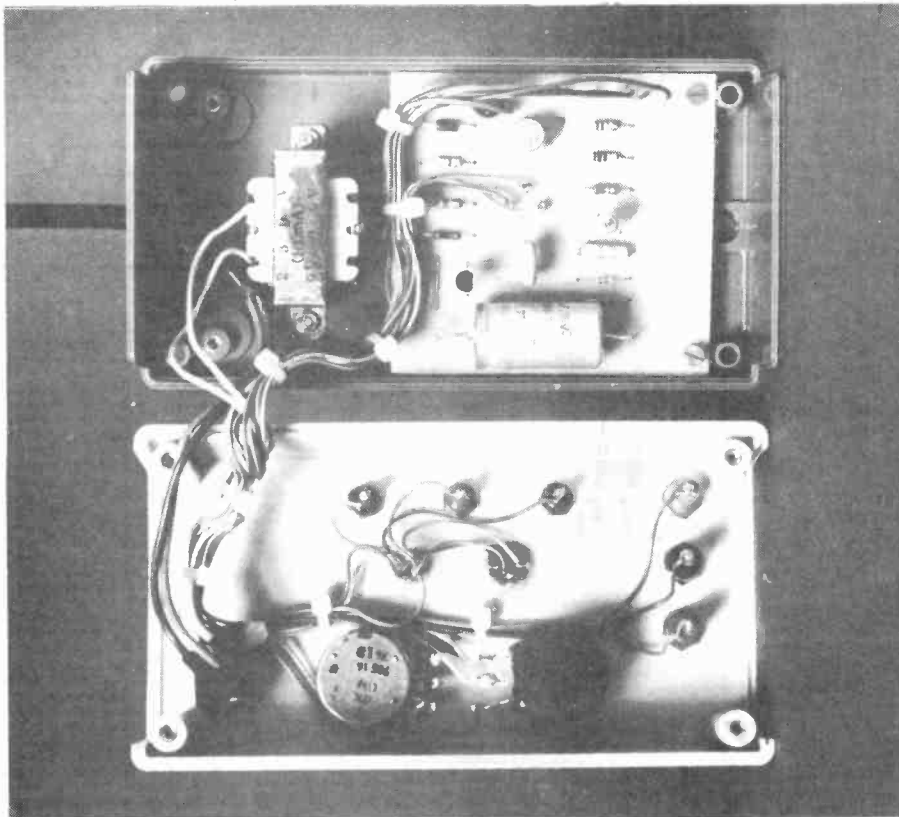View of the internal layout of the prototype version



Construction of the curve tracer is straightforward. Mount all the components on the PCB according to the overlay. The internal layout of our prototype is shown in the photographs. The unit is mains powered and a battery supply is not suitable for this circuit.

Initially try the curve tracer with a high gain nrn transistor, a BC108 will be ideal. Connect it to one of the tracer's sockets and connect the unit to the 'scope. Set the Y gain on the 'scope at maximum and set up the maximum required level of collector voltage by adjusting RV1. RV2 will control the number of steps displayed on the screen. The X sensitivity of the 'scope should be 1V per division.

The performance of the unit is degraded by the slight drop in the DC potential on C1 during the 10mS sweep and the slight effect of the 100R sampling resistor, in that its volt drop is included in the observed collector potential. However as stated above the unit will give a good indication of the dynamic performance of a wide range of semiconductor devices (as the photograph shows) at a price that is a fraction of similar commercial equipment.

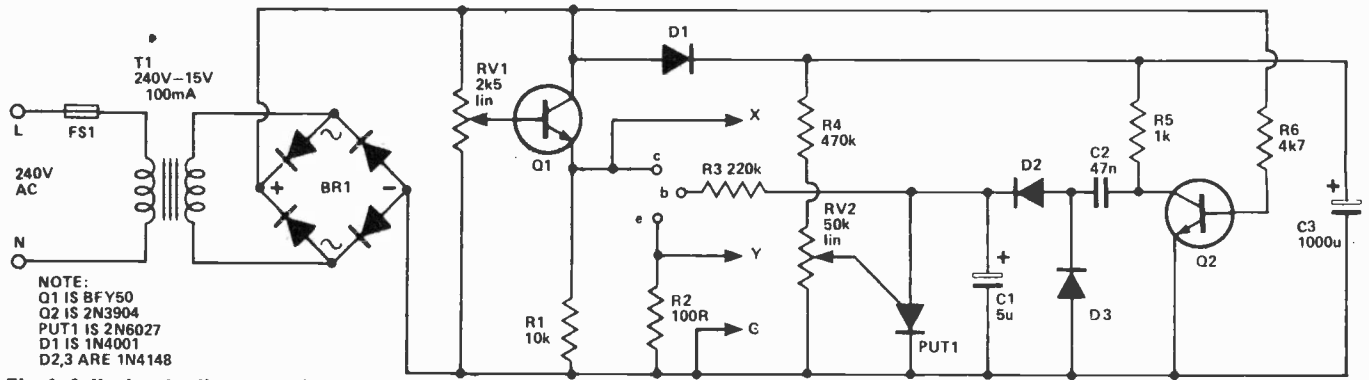


Fig. 1 full circuit diagram of the curve tracer.

HOW IT WORKS

The principles of the full circuit can perhaps be best explained by consideration of a simpler form of the circuit. Figs. 2 and 3 show circuits for investigating the dynamic characteristics of a diode and transistor (at fixed base current) respectively.

The 'diode circuit' will, unless an inverter is available, produce a trace that will appear upside down.

Operation of this circuit is quite straightforward. RV1 allows the peak value of the AC supply to be adjusted. This is then applied to the device under test via a current limiting resistor as well as to the X input of the scope. The current flow in the device at any time is proportional to the voltage developed across a low value sampling resistor in the current path. This voltage is fed to the Y input of the scope.

The simple transistor tester functions in much the same way. RV1 allows the base current to be adjusted within the range 10µA to 100µA.

The characteristics of an N-Channel FET (2N3819) may also be examined with this basic building block. The output characteristics are displayed for a gate voltage selected by RV1. Transfer characteristics (gate voltage vs. Drain Current) may be shown by transferring lead X to the gate terminal and mining the 1000µF capacitor to the 15V supply (observing the change in polarity).

Moving now to the full circuit of Fig 1 that allows a far more informative display providing, as it does, simultaneous displays of the characteristic curves for several equally spaced values of base current.

The circuit operates as follows. Every 10 ms the collector supply swings up and back over a half cycle of the full-wave rectified supply. At the end of each half cycle, there is a short period during which the supply potential is below about 0.6 V, and during this time, Q3 turns off, sending a pulse from its collector into the charge store C1 C2 D3 D2. Each pulse increases the potential in C1 by approximately 0.2 V. This would go on until the potential on C1 was 20 V were it not for Q2, the little known and much mis-described programmable unijunction transistor, PUT. This device is the semiconductor version of a neon lamp, insulating up to a certain p.d. and conducting heavily at potentials above this breakdown value, but with the added advantage in that, through a third terminal, this breakdown potential is programmable over quite a wide range. Varying this control potential through the setting of VR2 sets the

number of steps that will occur before the potential on C1 is great enough to make Q2 fire, reducing the capacitor's potential to approximately 0.6 V and so re-starting the sweep sequence.

The tracer can hardly be expected to match all the performance of a commercial curve tracer, the prices of which range into thousands of pounds. There are errors, due to the slight droop in d.c. potential on C1, and hence in base current, during the 10ms sweep, and due to the slight effect of the 100R sampling resistor, in that its volt drop is included in the observed collector potential, but as can be seen, these are quite insignificant as regards the final display. The only problem which may arise is the appearance of Radio 4 on the current axis (seen as a thickening of the trace). This is easily cured by placing a 10n disc capacitor across the actual Y-inputs of the oscilloscope.

A suitable transistor for the device under test is any reasonably high gain npn transistor, e.g. BC108. VR1 controls the maximum collector voltage, whilst VR2 sets the number of sweeps displayed. With the values given, the difference in base current between one step and the next is approximately given by:

$$\frac{1}{5R} \mu\text{A}, \text{ where } R \text{ is in megohms.}$$

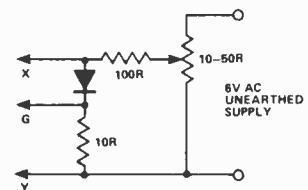


Fig. 2 simple diode tester

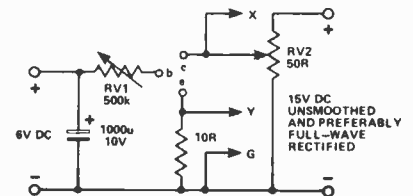


Fig. 3 fixed current transistor tester


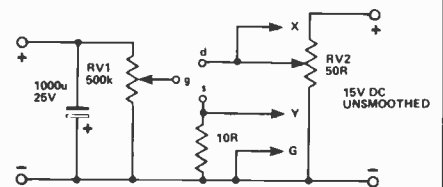


Fig. 4 circuit for investigating FET transfer characteristics.

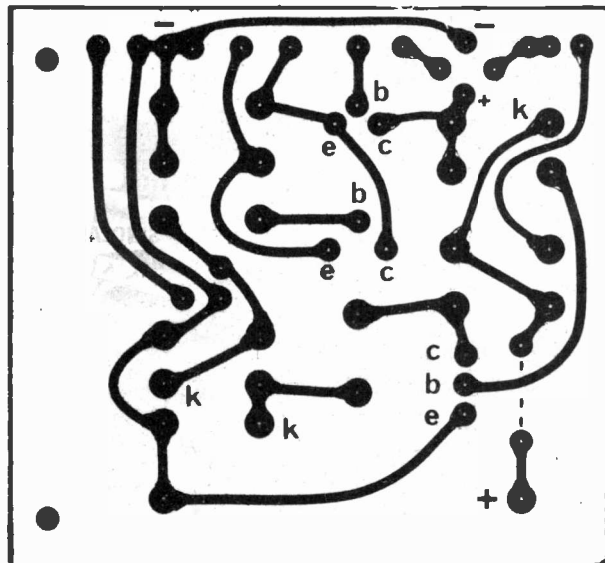

PARTS LIST

RESISTORS

R1	10k
R2	100R
R3	220k
R4	470k
R5	1k0
R6	4k7

CAPACITORS

C1	5u0 25 V electrolytic
C2	47n polyester
C3	1 000 25 V electrolytic

SEMICONDUCTORS

Q1	BFY50
Q2	2N3904
PUT1	2N6027
D1	1N4001
D2,3	1N4148
BR1	0.9A 400V

POTENTIOMETERS


RV1	2k5 1in
RV2	50k 1in

MISCELLANEOUS

PCB as pattern, case to suit, sockets, knobs, cable, etc.

BUYLINES

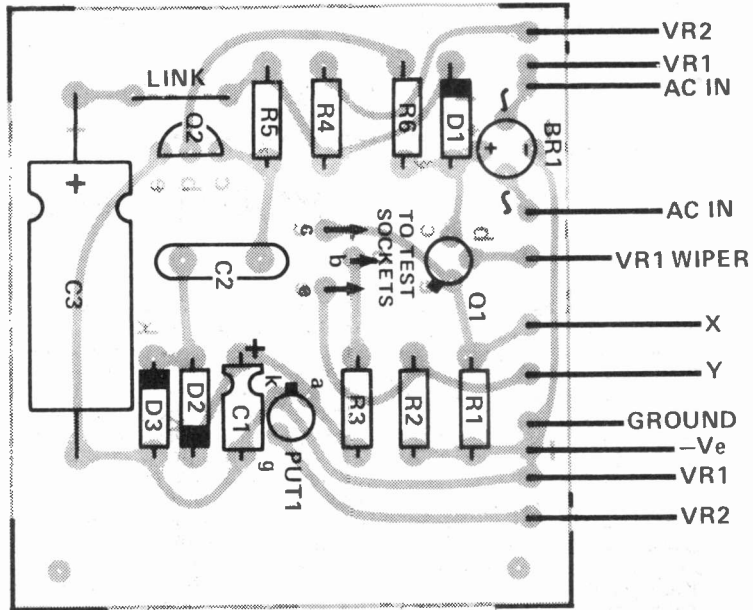The components used in this project should in the main, be generally available — the only component likely to cause problems is the PUT, but this should be available from the larger mail order outlets.



7400 TTL		74151		74522		74500			
7400	.10	74151	.58	74522	.38	74500	.18		
7401	.12	74154	1.00	74527	.38	2N3053	.20		
7402	.12	74156	.60	74551	.26	2N2054	.57		
7403	.12	74157	.54	74564	.20	2N3055	.57		
7404	.10	74160	1.04	74574	.38	2N3752	.12		
7406	.27	74162	.80	745112	.56	2N3754	.12		
7406	.27	74163	1.18	745124	3.25	2N3819	.29		
7406	.12	74164	.87	MICRO'S				DIODES	
7409	.13	74165	.93	MEMORIES				8AX13	.05
7410	.12	74175	.67	745186	2.40	1N914	.05		
7411	.21	74176	.84	7472A	3.99	1M4148	.05		
7412	.21	74180	.86	2706	7.96	1M4151	.04		
7413	.24	74190	1.04	2702-1	1.22	1N4001	.06		
7471	.64	74192	.98	2714	10.53	1N4002	.06		
7416	.26	74193	.98	8080A	7.02	1N4003	.08		
7417	.33	74194	.86	8251	.70	1N4004	.10		
7420	.12	74196	.86	8251	.70	1N4005	.11		
7426	.24	74197	.86	LINEAR				1N4005	.11
7427	.24	74198	1.41	LM3900	.4R	1N4007	.12		
7430	.12	74 LS TTL		LM741-8	.21	1N4500	.16		
7432	.23	74LS00	.18	NE555	.29	1N4500	.16		
7433	.50	74LS01	.18	NE555	.29	ELECTROLYTICS			
7437	.23	74LS02	.18	NE556	.71	UF/V			
7438	.23	74LS04	.19	NE565	1.14	47/100	.08		
7440	.16	74LS05	.21	NE567	1.62	1/63	.08		
7441	.50	74LS08	.21	REGULATORS		2/253	.08		
7442	.38	74LS09	.21	7805	.80	3/353	.08		
7443	.85	74LS10	.21	7812	.80	4/753	.08		
7445	.67	74LS11	.21	7905	1.39	10/16	.08		
7446	.67	74LS14	1.10	7912	1.39	10/35	.08		
7447	.59	74LS20	.18	LM309	.86	10/63	.09		
7448	.48	74LS21	.21	LM723	.38	22/15	.08		
7450	.16	74LS22	.24	AC TRANSISTORS		22/25	.10		
7451	.16	74LS27	.26	AC128	.23	22/63	.12		
7453	.16	74LS38	.29	AC176	.23	33/16	.08		
7454	.16	74LS40	.25	AC107	.10	33/35	.11		
7450	.16	74LS42	.54	BC108	.10	33/63	.13		
7470	.36	74LS51	.29	BC109	.10	47/16	.09		
7472	.32	74LS74	.32	BC177	.18	47/25	.12		
7473	.21	74LS86	.33	BC178	.18	47/63	.15		
7474	.26	74LS90	.66	BC179	.18	100/16	.11		
7475	.29	74LS93	.86	BC184	.15	100/35	.13		
7476	.31	74LS107	.34	BFY50	.23	100/63	.24		
7483	.68	74LS112	1.00	BFY52	.23	220/16	.12		
7485	.84	74LS123	.85	BFY52	.23	220/16	.17		
7486	.25	74LS124	2.20	BFY52	.23	470/16	.18		
7489	1.95	74LS151	.95	BFY52	.23	470/25	.38		
7490	.38	74LS153	.64	BFY52	.23	1000/16	.30		
7491	.62	74LS157	.64	BS195A	.17	1000/25	.48		
7482	.42	74LS164	.42	OC71	.20	2200/16	.54		
7493	.29	74LS175	1.05	OC200	.45	BURROUGHS 9 Dig.			
7495	.51	74LS193	1.33	TIP 2955	.85	7 Seg. Panalux Display.			
7496	.67	74LS194	2.06	TIP 3055	.68	0.25" Neon Type with			
74104	.48	74S TTL		TI843	.33	Red Bezel and Socket.			
74105	.48	74S TTL		TI8300	.17	€2.25			
74107	.27	74S04	.26						
74109	.45	74S05	.38						
74111	.29	74S08	.38						
74122	.47	74S10	.38						
74123	.38	74S12	.38						
74141	.71	74S18	.38						

All prices INCLUDE V.A.T. add 25p P&P

IBEX SYSTEMS
32 Dunville Drive, Coventry CV2 2HS

THE SINCLAIR PDM35 digital Multimeter

Now a digital multimeter at an analogue price and look at the spec!

D.C. VOLTS 1mv-1000v(1% — 1 count) 10mΩ input.

A.C. VOLTS 1v-500v, 40Hz-5kHz (1% + 2 counts).

D.C. CURRENT 1 inA-200mA (1% count).

RESISTANCE 1Ω-20mΩ (1.5% + 1 count).

£29.80 cash with order or £30.95 company purchase order.
Adaptor £3.20. Padded case £3.20 30kV probe £18.64

THE SINCLAIR MICROVISION

The amazing pocket T.V. that will pick up programs throughout the world, complete with rechargeable batteries.

£189.95 inc. VAT
See (for detailed Brochure ex-stock)

SINCLAIR DM235

Portable 3 1/2 digit 6 function Multimeter
DC volts 1mV to 1000V
AC volts 1mV to 750V
AC & DC current 1μA to 1A
Resistance (Ω to 20MΩ)
Diode test 0.1μA to 1mA
10mΩ input. DC acc 1.0% AC acc 1.5% 30Hz-10kHz

Cash with order
£52.80 inc VAT or £53.70 on company purchase order

PORTABLE ALARM CLOCK

Only **£18.20** inc. P&P

- Battery operated
- Quartz crystal accuracy
- Back light
- Simple to set
- Electric Alarm
- Snooze button
- Colour Rinwn

CA-OBAL
Case £8.95 Adaptor £3.75

We accept govt / company purchase orders on all goods

KRAMER & CO

We will match any lower advertised price on a cash with order basis if competitor has goods in stock

9 October Place, Holders Hill Road, London NW14 1EJ
Tel: 888941 Attn. Kramer K7. Tel. 01-203 2473
Mail order only SAE for data sheets Export enquiries welcome

ETCH RESIST TRANSFER KIT SIZE 1:1

Complete kit 13 sheets 6in x 4 1/2in **£2.50** with all symbols for direct application to P.C. board. Individual sheets 25p each. (1) Mixed Symbols (2) Lines 0.05 (3) Pads (4) Fish Plates and Connectors (5) 4 Lead and 3 Lead and Pads (6) DILS (7) BENDS 90 and 130 (8) 8-10-12 T.O.5. Cans (9) Edge Connectors 0.15 (10) Edge Connectors 0.1 (11) Lines 0.02 (12) Bends 0.02 (13). Quad in Line.

FRONT AND REAR PANEL TRANSFER SIGNS

All standard symbols and wording. Over 250 symbols, signs and words. Also available in reverse for perspex, etc. Choice of colours, red, blue, black, or white. Size of sheet 12in x 9in. Price: **£1**.

GRAPHIC TRANSFERS WITH SPACER ACCESSORIES

Available also in reverse lettering, colours red, blue, black or white. Each sheet 12in. x 9in contains capitals, lower case and numerals 1/8in kit or 1/4in kit. **£1** complete. State size.

All orders dispatched promptly.
All post and VAT paid.
Ex U.K. add 50p for air mail
Shop and Trade enquiries welcome
Special Transfers made to order

E. R. NICHOLLS
P.C.B. TRANSFERS
Dept. HE/1
46 LOWFIELD ROAD
STOCKPORT, CHES.061-480 2179